


# EIE2050 Digital Logic and Systems

## Project: Serial-in-parallel-out shift register

### ■ Objectives and Aims:

- Get familiar with the hardware programming language VHDL
- Study the use of different architectural design methods
- Study the use of combinational and sequential logics
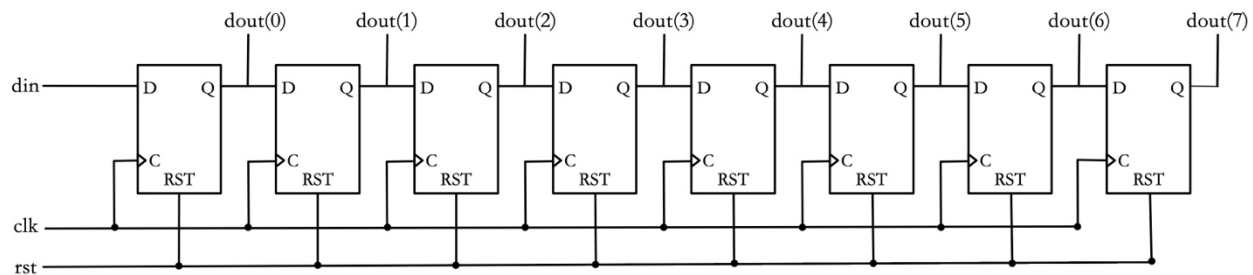
### ■ Exercise: In this lab, you need to implement a **serial-in-parallel-out (SIPO) shift register**, which is composed of **8 D-Flip-Flops (D-FF)** as follows:




- The SIPO shift register allows serial input (one bit after the other through a single data line **din**) and produces a parallel output (through **dout(0)** to **dout(7)**).
- When **rst** equals to 1, all the **dout(s)** are reset to be zero.
- Otherwise (when **rst** equals to 0), at every rising edge of **clk**, the signal of **din** is shifted into the “leftmost” D-FF; meanwhile the signal kept by each D-FF is shifted to the D-FF on its right; and the signal kept by the “rightmost” D-FF is shifted out from the SIPO shift register.

### ■ Requirements:

- Implement a serial-in-parallel-out (SIPO) shift register, which is composed of 8 D-Flip-Flops (D-FF), using the **structural design (port map)**.
  - That is, implement the D-Flip-Flop first, and then use D-Flip-Flop to implement the SIPO shift register.
  - Write down a testbench to verify the SIPO function (waveform diagram). An input waveform diagram as below is provided for

reference. Note that the **clk**'s rising edge should be before the **rst**'s falling edge to eliminate uncertain outputs (U).

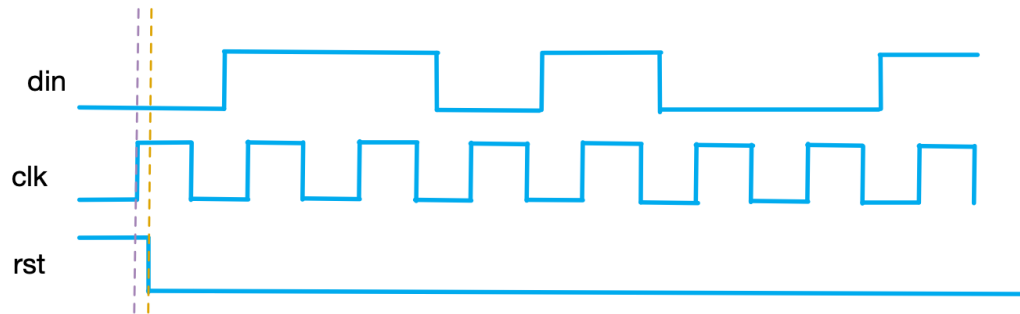clk's rising edge is before the rst's falling edge



- Submission Rule:
  - Submit your (1) source code(s) (.vhd), (2) testbench (.vhd), and (3) the behavior simulation result (a screen shot) to BB
- Deadline: April 19, 2023